 


## Assignment 5

### Due November 19, 12:59pm

**NOTE:** Late submissions will **NOT** be accepted. Please put your solutions in the CENG 355 **drop-box** (ELW, second floor) – they will be collected at **13:00**.

1. [10 points] Solve Problem **7.11** from the textbook.
  
2. [5 points] Consider the following Slave's protocol in some handshake scenario: (1) Slave waits for Master to assert signal *REQ*; (2) Once *REQ* is received, Slave asserts signal *WAIT* for two clock cycles; (3) Once the two clock cycles have elapsed, Slave de-asserts *WAIT* and waits for Master to de-assert *REQ*; (4) Once *REQ* is removed, Slave goes back to step (1). Show the Moore FSM state diagram for this protocol. **Note:** *WAIT* is asserted only in step (2).
  
3. [5 points] Recall the Mealy FSM state diagram on **Slide 41** of the “**Interfacing**” lecture notes, where the circuit is initially in state **Idle**. Given the input waveform shown below, draw the corresponding output waveforms.



4. [5 points] Consider the daisy-chain arbitration scheme shown below. Assume that the input-to-output signal propagation delays are the same and equal to **d** for all three devices, the inverter, and the **AND** gate. Also, assume that device **x** is able to start using the bus (making  $\text{BR}_x = 1$  and  $\text{BBSY} = 0$ ) only when it receives a 0-1 transition on its bus-grant input **BGx** and detects that the bus is not currently busy (i.e.,  $\text{BBSY} = 1$ ). Also, assume that device **x** lets the bus-grant propagate through only when it is neither requesting nor using the bus. Finally, assume that any of the three devices will need to use the granted bus for only **3d** time units. Complete the timing diagram shown below, where Device 2 requests the bus at time **t = 0**, and Device 3 requests the bus at time **t = 3d**.

