

Interfacing

D.N.Rakhmatov

Adopted (with modifications) from:

R. Katz, UC-Berkeley

F. Vahid, UC-Riverside

D. Givone, SUNY-Buffalo

J. Armstrong, Virginia Tech

C. Hamacher et al, *Computer Organization*, 6/E, © 2011 McGraw-Hill


S. Dandamudi, *Fundamentals of Computer Organization and Design*, © 2002 Springer

Fall 2016

UVic - CENG 355 - Interfacing

1

System Integration

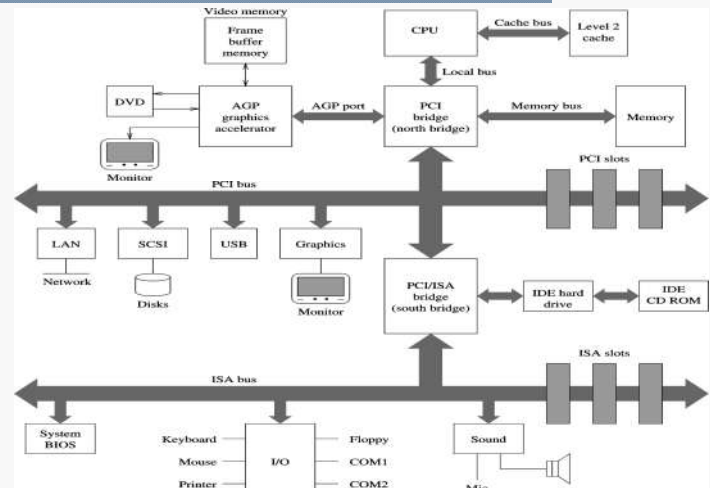

Fall 2016

UVic - CENG 355 - Interfacing

2

System Bus I

- Bus = address + data + **control** (command/status)
- Some typical control bus signals:
 - Memory read/write
 - This includes **memory-mapped I/O** read and write
 - For **isolated I/O**, need an extra signal indicating address type
 - Interrupt-Request, Interrupt-Acknowledge
 - Address-Valid, Data-Valid, Master-Ready, Slave-Ready
 - Bus-Request, Bus-Grant, Bus-Busy
 - Clock, Reset, Enable, Wait
- Bus **master** – the device that is allowed to initiate bus transactions at any given time
 - Only **one** master at a time, everyone else is a **slave**
 - Bus mastership can be changed through bus **arbitration**

Fall 2016

UVic - CENG 355 - Interfacing

3

System Bus II

- General bus operation:
 - Master places desired slave's address onto address bus
 - All slaves must examine the address and decide if they are being referenced (address decoding)
 - Master (or selected slave) places data onto data bus for a write (read) operation
 - Selected slave (or master) gates the data into its internal registers to complete the operation
 - Operation is directed by the control bus signals
- Bus is **NOT** a static connection mechanism
 - Devices must be enabled (given access to write to the bus) only when they are participating in a data transfer
 - Only **one** device may drive the bus at any given time
 - Other devices should be in high-impedance state

Fall 2016

UVic - CENG 355 - Interfacing

4

Synchronous Bus


- In a synchronous bus, the timing of all devices is synchronized to the **bus clock**
 - Delay issues:
 - Certain delays are introduced by the bus drivers that place new information on the address or data lines
 - An additional delay is encountered as information propagates along the bus wires
 - The receiving end requires a certain (minimum) amount of setup time to latch the incoming data correctly
- Example: **Read** operation
 - At the rising clock edge (**t₀**) – the master places the device's address on the bus address lines
 - At the falling clock edge (**t₁**) – the slave responds by placing its data on the bus data lines
 - At the next rising clock edge (**t₂**) – the master latches the data on the bus data lines into its input buffer

Fall 2016

UVic - CENG 355 - Interfacing

5

Synchronous Read Example

 


1. (**t₁ – t₀**) must be longer than the maximum propagation delay between the master and the slave, plus the slave's delay of decoding the address and control signals
2. (**t₂ – t₁**) must be longer than the maximum propagation delay between the master and the slave, plus the master's setup time

Fall 2016

UVic - CENG 355 - Interfacing

6

More Detailed Picture (Read)

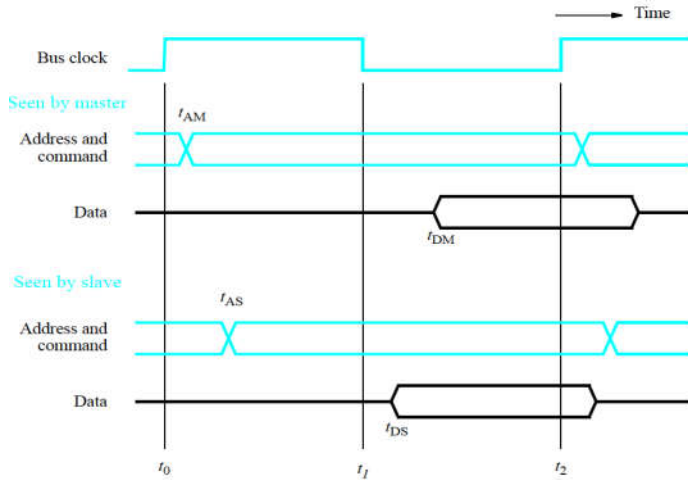

Fall 2016

UVic - CENG 355 - Interfacing

7

Multi-Cycle Bus Transfers


- **Single-cycle** bus transfer mechanism forces all devices to operate at the speed of the slowest one
 - Also, the master cannot determine if the selected slave has responded correctly
- **Multi-cycle** bus transfers increase bus utilization and transfer reliability
 - Example: multi-cycle read operation
 - ↑ **Cycle 1** – master puts the slave's address and command on the bus, along with the (OPTIONAL) **master-ready** signal
 - ↑ **Cycle 2** – slave decodes this information and accesses the requested data
 - ✓ This step may take more than one clock cycle, delaying subsequent steps
 - ↑ **Cycle 3** – slave puts the ready data on the bus and asserts the (REQUIRED) **slave-ready** signal
 - ↑ **Cycle 4** – the master receives this information and latches the data into its input buffer

Fall 2016

UVic - CENG 355 - Interfacing

8

Multi-Cycle Read Example

 


Fall 2016

UVic - CENG 355 - Interfacing

9

More Examples: Read, no Wait

 


Fall 2016

UVic - CENG 355 - Interfacing

10

More Examples: Read, with Wait

 


Fall 2016

UVic - CENG 355 - Interfacing

11

More Examples: Block Read

 

Fall 2016

UVic - CENG 355 - Interfacing

12

Asynchronous Bus


- In an asynchronous bus, the clock becomes optional and is replaced by two REQUIRED signals, **Master-ready** and **Slave-ready**
 - The clock may still be present, but only as a reference
- **Handshake** idea:
 - The master places the address and command on the bus and asserts **Master-ready**
 - All devices on the bus decode the address
 - The selected slave performs the requested operation and asserts **Slave-ready**
 - The master waits for **Slave-ready** to be asserted before removing its signals from the bus
 - Once **Master-ready** is deasserted, the slave removes its signals from the bus

Fall 2016

UVic - CENG 355 - Interfacing

13

Asynchronous Read Example

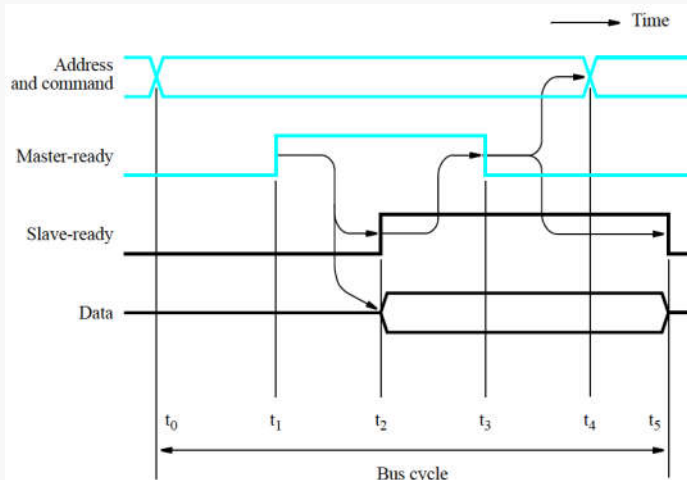


Fall 2016

UVic - CENG 355 - Interfacing

14

Asynchronous Write Example

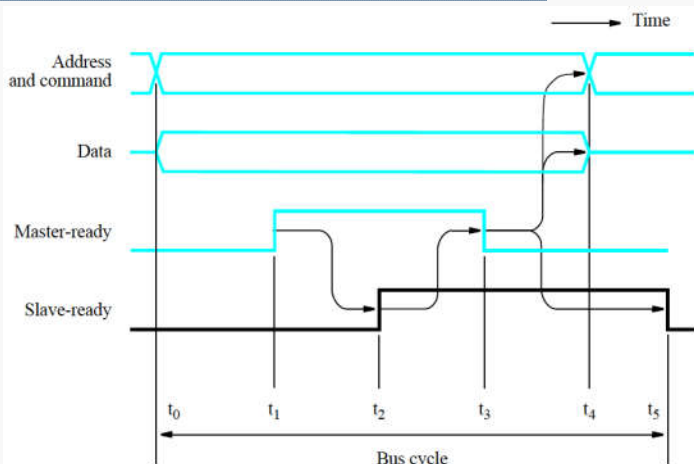

Fall 2016

UVic - CENG 355 - Interfacing

15

More on Asynchronous Bus

- Bus design tradeoffs:
 - Simplicity of the device interface circuit
 - Total time required for a bus transfer
 - Ability to accommodate devices with different delays
 - Ability to detect errors during a transfer
- Asynchronous bus advantages
 - No need for a synchronizing clock = simpler timing
 - Insensitivity to device delay variations
 - High degree of flexibility and reliability
- Asynchronous bus disadvantages
 - Fully interlocked handshaking involves two round-trip delays per each transfer
 - **Master-ready** must wait for **Slave-ready** and vice versa


Fall 2016

UVic - CENG 355 - Interfacing

16


Protocol Concepts (e.g., Read)

Strobe Protocol

 

1. Master asserts **req** to receive data
2. Slave puts data on bus within time t_{access}
3. Master receives data, deasserts **req**
4. Slave is ready for next request

Handshake Protocol

 


1. Master asserts **req** to receive data
2. Slave puts data on bus, asserts **ack**
3. Master receives data, deasserts **req**
4. Slave stops driving bus, deasserts **ack**
5. Slave is ready for next request

Fall 2016


UVic - CENG 355 - Interfacing

17

Strobe/Handshake Compromise

 


Fast-response case

 

1. Master asserts **req** to receive data
2. Slave puts data on bus within t_{access} (**wait** is unused)
3. Master receives data, deasserts **req**
4. Slave is ready for next request

Slow-response case

 

1. Master asserts **req** to receive data
2. Slave cannot put data within t_{access} , it asserts **wait**
3. Slave puts data on bus, deasserts **wait**
4. Master receives data, deasserts **req**
5. Slave stops driving bus
6. Slave is ready for next request


Fall 2016

UVic - CENG 355 - Interfacing

18

Bus Arbitration

- **Bus arbitration** – the process of determining which device is to become the next bus master and then transferring the mastership to it
 - Need a priority scheme for gaining access to the bus
- Two approaches: **distributed** (all devices are involved) and **centralized** (similar to interrupts)

 

Fall 2016

UVic - CENG 355 - Interfacing

19

Distributed Arbitration I

- All devices are responsible for carrying out the arbitration process, without using a central arbiter
- Example:
 - Each device has its 4-bit **ID**, which is put on the bus control lines with asserted signal **Start-Arbitration** (when requesting a bus access)
 - A winner is selected as a result of the interaction among the signals transmitted by all current contenders
 - Assume devices **A** (**ID=5**) and **B** (**ID=6**) are requesting the use of the bus
 - **A** puts **0101** and **B** puts **0110** – the open-collector (o.c.) driven lines will be at state **0111** (i.e., logical OR of **0101** and **0110**)
 - **A** and **B** compare **0111** to their **IDs** starting from the MSB
 - **A** detects a mismatch earlier and disables its **ID** drivers, thus making the lines change their state to **0110** – **B** wins!


Fall 2016

UVic - CENG 355 - Interfacing

20

Distributed Arbitration II

- Let device's **ID** be stored in its **Priority Register**
 - **1111** means the highest priority, **0000** – the lowest
 - If a device wins, it asserts its output **Winner**

 


Fall 2016

UVic - CENG 355 - Interfacing

21

Centralized Arbitration I

Priorities: BR1 > BR2 > BR3

 


Fall 2016

UVic - CENG 355 - Interfacing

22

Centralized Arbitration II

 


Fall 2016

UVic - CENG 355 - Interfacing

23

Hybrid Daisy Chain

- Devices are divided into **N** classes
- Each class has independent bus-request with bus-grant
- Devices within the same class form a daisy chain

 


Fall 2016

UVic - CENG 355 - Interfacing

24

Daisy Chain Example I

 



Ignoring propagation delay on wires, assume that the inverter delay is d_{inv} , and the delay from BG_k to BG_{k+1} for any device is $d > d_{inv}$. Assume that device 3 requests the bus and begins using it; when finished, device 3 deactivates BR_3 . As a result, a spurious (unwanted) bus grant pulse will travel down the daisy chain.

Fall 2016

UVic - CENG 355 - Interfacing

25

Daisy Chain Example II

  


Fall 2016

UVic - CENG 355 - Interfacing

26

Daisy Chain of DMA Controllers

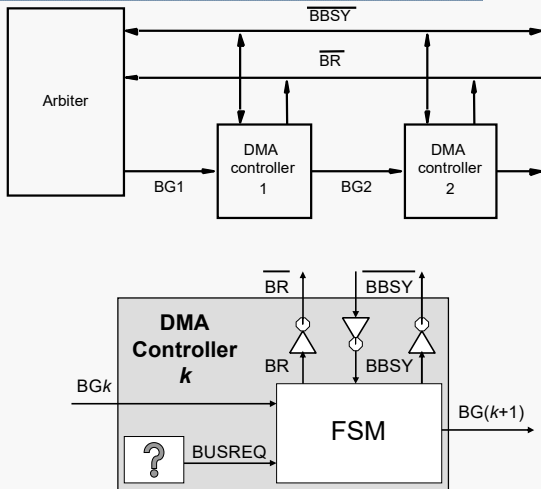


Fall 2016

UVic - CENG 355 - Interfacing

27

FSM State Diagram

Inputs / Outputs = BUSREQ, BGk, BBSY / BR, BG(k+1), BBSY

 


Fall 2016

UVic - CENG 355 - Interfacing

28

FSM Waveform Example

 


Fall 2016

UVic - CENG 355 - Interfacing

29

FSM Design

- FSM design procedure
 - Determine state diagram (your **design**)
 - Encode states
 - Implement next-state logic and output logic
- Mealy (a) and Moore (b) FSMs
 - Mealy**: output depends on input, one cycle faster
 - Moore**: output does not depend on input, more reliable

 


Fall 2016

UVic - CENG 355 - Interfacing

30

Moore ASM Chart

 


Fall 2016

UVic - CENG 355 - Interfacing

31

Mealy ASM Chart

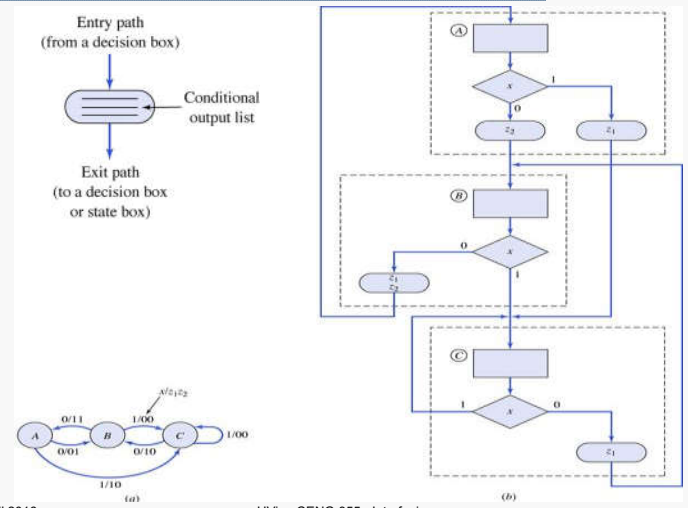

Fall 2016

UVic - CENG 355 - Interfacing

32

I/O Interface Circuits


- Basic I/O interface functions:
 - Contains **address decoding** circuitry that detects when the I/O device is being addressed
 - Generates the appropriate signals required for **bus control**
 - Provides a buffer for temporary **data storage**
 - Contains **status flags** that can be accessed to determine whether the buffer is full (input) or empty (output)
 - Performs necessary **data format conversions** between the bus and the I/O device (e.g., serial-to-parallel conversion)
- The interface circuit classifies the I/O device as either serial or parallel port

Fall 2016

UVic - CENG 355 - Interfacing

33

Serial I/O Interface

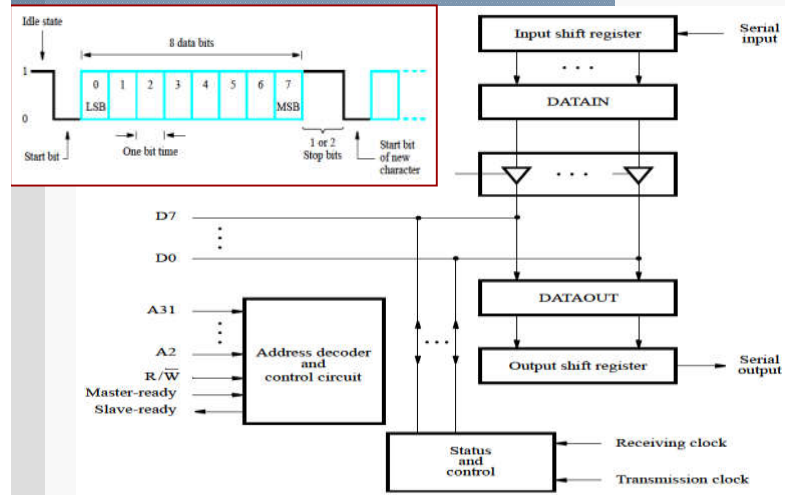


Fall 2016

UVic - CENG 355 - Interfacing

34

Example: Parallel Ports

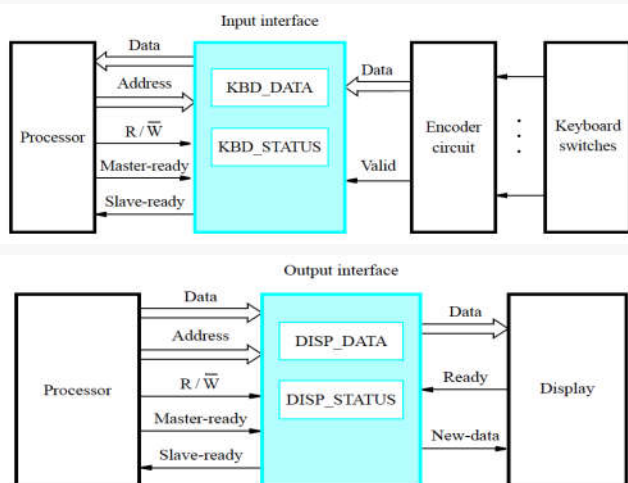


Fall 2016

UVic - CENG 355 - Interfacing

35

Example: Interface Registers

 


Fall 2016

UVic - CENG 355 - Interfacing

36

Parallel Input Interface I

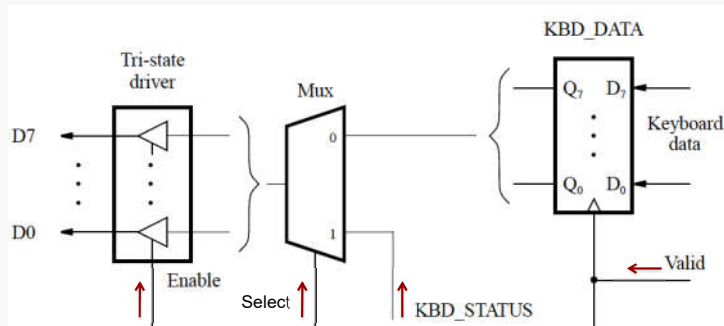


Fall 2016

UVic - CENG 355 - Interfacing

37

Parallel Input Interface II

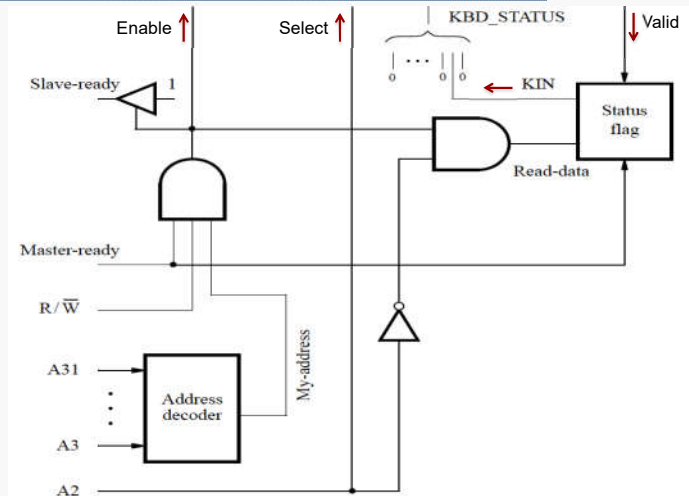


Fall 2016

UVic - CENG 355 - Interfacing

38

Status Flag Control

KIN is set by **Valid** (when **Master-ready** is not asserted) and cleared by **Read-data** (when **Master-ready** is asserted)...

 


Fall 2016

UVic - CENG 355 - Interfacing

39

Parallel Output Interface

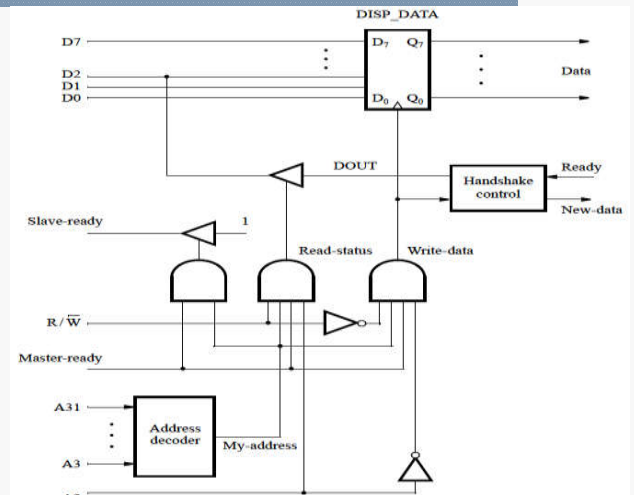


Fall 2016

UVic - CENG 355 - Interfacing

40

Synchronous Interfacing I

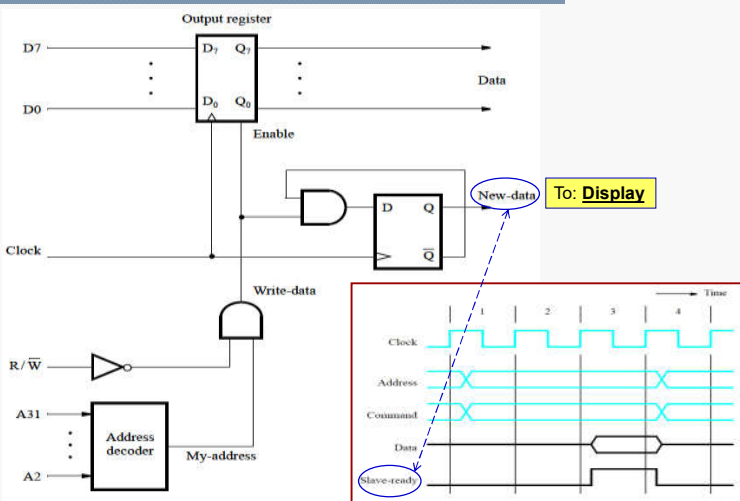


Fall 2016

UVic - CENG 355 - Interfacing

41

Synchronous Interfacing II

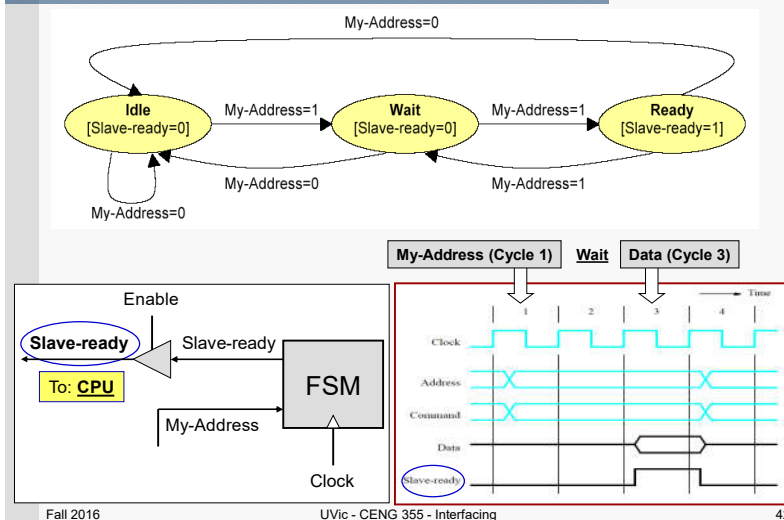

Fall 2016

UVic - CENG 355 - Interfacing

42